Resistive switching and memory computing


A resistive memory cell typically has a top electrode, switching layer and bottom electrode. A programming pulse changes its stored state; a specified read bias probes its current.

LRS and HRS mean low and high resistance. Assigning either state to a binary value is a system convention, not a material law. We connect measurements to physical models, arrays and reliability without treating one observation as proof of a unique mechanism.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Cell structure and voltage reference

Two-terminal cell: define voltage first

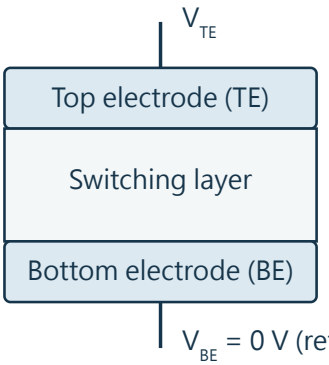

Define $V = V_{TE} - V_{BE}$

Operations and readout

SET: higher conductance

RESET: lower conductance

Read: state voltage and duration

$G_{read} = I_{read} / V_{read}$

Polarity and current limit are device-specific; no particular mechanism is assumed.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Read conductance has measurement conditions

At a specified voltage and time, define $G_{read} = I_{read}/V_{read}$. This ratio is an apparent conductance at that operating point.

Nonlinear response, polarity asymmetry or drift can make it different at another bias or time. A read can also disturb the stored state.

A voltage sweep traces a response under a specified sweep rate and current limit. Pulse experiments specify amplitude, duration and sequence and can probe switching and read disturbance.

Report temperature, voltage polarity, compliance, pulse timing and read protocol. A single curve does not establish device-to-device or cycle-to-cycle distributions.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Forming, SET, RESET and read

- Forming is an initial conditioning step required by some devices, not all.
- SET generally moves to a more conductive state; RESET moves to a less conductive state.
- Read probes the state. Current compliance constrains programming current but does not guarantee freedom from damage.

For bipolar switching, SET and RESET generally use opposite bias polarities. Unipolar switching can use the same polarity with different pulse or current-limit conditions.

Define voltage explicitly, for example $V = V_{top} - V_{bottom}$, before naming positive or negative. A polarity observed in one stack is not universal.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Trace a pulse protocol

This synthetic example assumes a particular bipolar stack and $V = V_{top} - V_{bottom}$; the numbers are illustrative, not specifications. Record the read immediately after each pulse and again later to detect drift.

Step	Applied pulse	Current limit	Read at 0.1 V	Inference
Initial read	+0.1 V, 10 µs	read circuit	1 µA	$G_{read} = 10$ µS
SET	+1.0 V, 1 µs	100 µA	20 µA	$G_{read} = 200$ µS
RESET	−1.0 V, 1 µs	not specified	1 µA	$G_{read} = 10$ µS


Compliance constrains programming current; a low read pulse is not automatically nondestructive. Verify repeated reads and record drift instead of inferring it from one measurement.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Pulse operations and state sequence

Pulse and read sequence: illustrative example

Example only; V = Vtop − Vbottom.

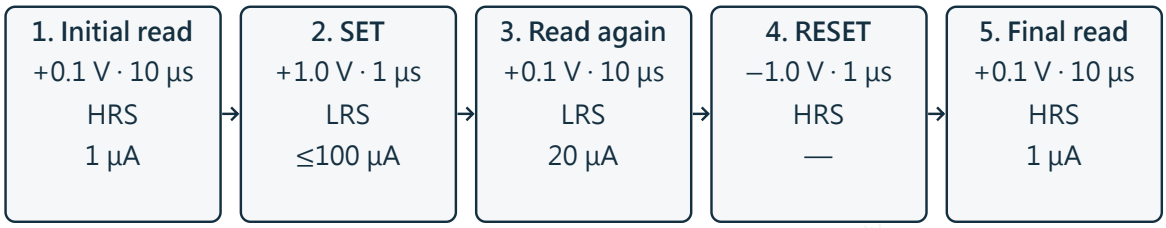

Read currents shown; SET limited; RESET current unspecified.
Not to scale; reads assumed nondisturbing.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

ECM: a possible redox pathway


In electrochemical metallization (ECM), an active electrode can oxidize; metal cations migrate through the switching layer and reduction can form a conductive bridge. Subsequent operation can narrow or rupture it.

For a hypothetical Ag / oxide / inert-electrode stack with Ag positive during SET, oxidation $\mathrm{Ag} \rightarrow \mathrm{Ag}^{+} + e^{-}$ supplies cations while electrons enter the external circuit. Reduction $\mathrm{Ag}^{+} + e^{-} \rightarrow \mathrm{Ag}$ can deposit metal where electrons are available.

Nucleation, growth direction and RESET depend on electron supply, transport and reaction kinetics. This polarity and schematic are examples, not universal rules.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

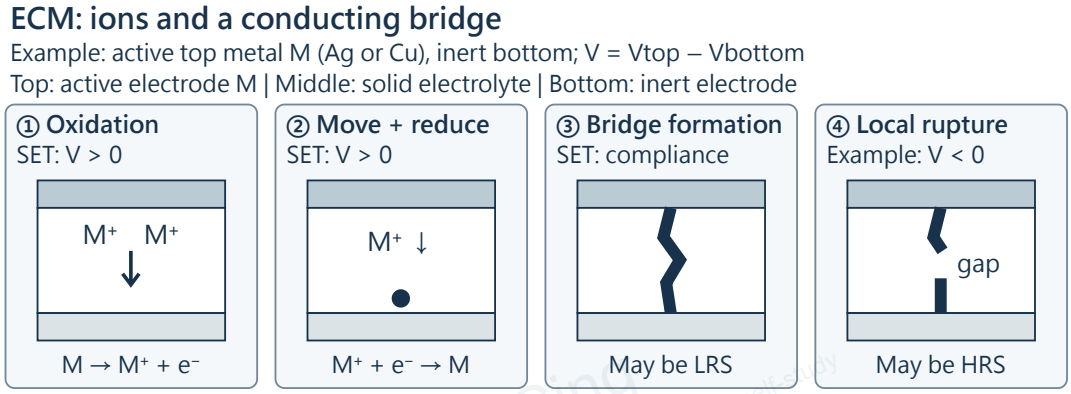ECM stages for one electrode configuration



Schematic, not to scale; growth direction depends on materials and reaction kinetics.
RESET polarity, rupture location and pulse depend on device; specify read conditions.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study


VCM and competing explanations

Valence-change mechanisms (VCM) involve oxygen-ion or oxygen-vacancy transport and local redox changes. Redistribution changes local stoichiometry and electronic transport. One model emphasizes a filament; another emphasizes an interface barrier. Each requires specific electrode, field and redox assumptions. Thermochemical contributions and unipolar behavior are not universally equivalent.

A hysteretic I–V curve is not proof of a unique mechanism. Local chemical maps, conductive microscopy, in-situ imaging and time-resolved measurements can test models, subject to resolution and possible measurement perturbations; correlation alone does not establish causality.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Two candidate VCM models

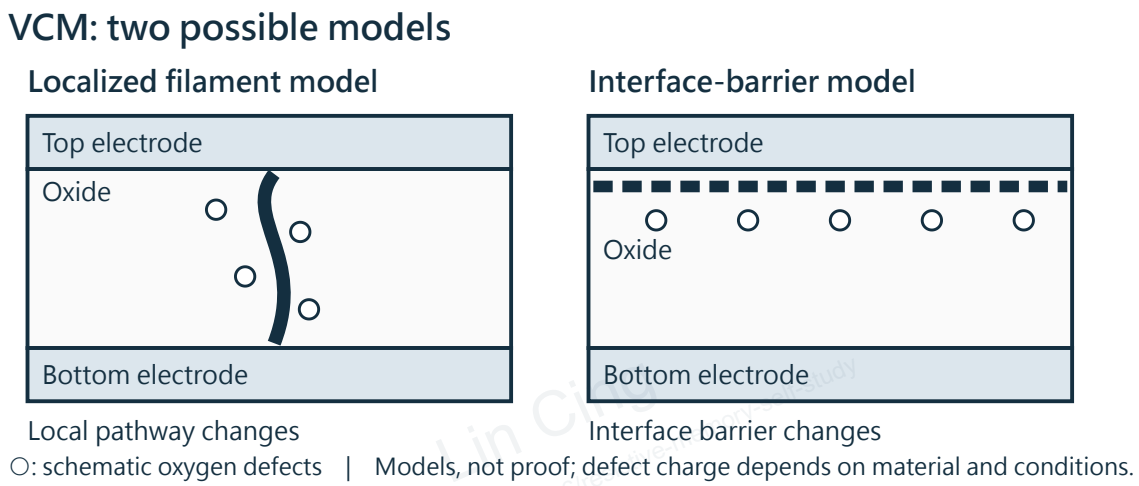

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Model a state without assuming a mechanism

One framework is $i(t) = G(x(t), v(t), t)v(t)$ and $\dot{x} = f(x, v, t)$. The chosen state x may be multidimensional, and G need not be independent of voltage or time.

An ideal memristor is not synonymous with every two-terminal device displaying hysteresis. A model must state its domain and be tested against measurements.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

An ideal crossbar computes column currents

Let row i be driven at V_i and the conductance at row i, column j be G_{ij}. Assume linear read response, negligible wire resistance, and columns held at virtual ground.

Each branch carries $I_{ij} = G_{ij}V_i$. Kirchhoff's current law then gives $I_j = \sum_i G_{ij}V_i$. These assumptions are part of the result.

For $G = \begin{bmatrix} 2 & 1 \\ 1 & 3 \end{bmatrix}\ \mu\mathrm{S}$ and $V = (0.2, 0.1)\ \mathrm{V}$, the two column currents are $I_1 = 2(0.2) + 1(0.1) = 0.5\,\mu\mathrm{A}$ and $I_2 = 1(0.2) + 3(0.1) = 0.5\,\mu\mathrm{A}$. Here $\mu\mathrm{S} \cdot \mathrm{V} = \mu\mathrm{A}$; the numbers illustrate the model.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Derive the array sum at the cell terminals


Let the local row and column potentials at cell (i, j) be v_{ij} and u_{ij}. For a linear read conductance, the branch current into the column is $I_{ij} = G_{ij}(v_{ij} - u_{ij})$. Kirchhoff's current law sums these branch currents at the column sensing node. Only when row wires are ideal and the column is held at virtual ground do $v_{ij} = V_i$ and $u_{ij} = 0$ yield $I_j = \sum_i G_{ij} V_i$.

With the earlier 2×2 example, suppose both local row-2 potentials are 0.08 V, row 1 remains 0.2 V, and column potentials remain zero. Then $I_1 = 2(0.2) + 1(0.08) = 0.48$ µA and $I_2 = 1(0.2) + 3(0.08) = 0.44$ µA. This assumes the local voltages are known; solving a real resistive network determines them rather than prescribing them.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Ideal crossbar: two input rows

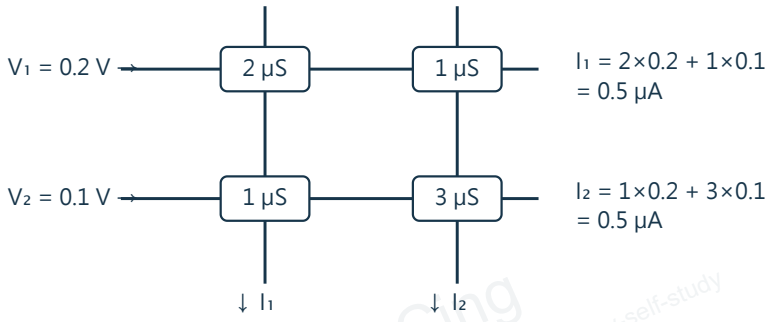2 × 2 crossbar: sum branch currents by column



Assumptions: linear read, no wire resistance, virtual-ground columns.
$I_j = \Sigma_i G_{ij} V_i$; units: µS × V = µA.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

When the array differs from the model

Wire resistance changes local voltages; finite sensing impedance changes column potential. Leakage, unintended paths, nonlinear response, conductance drift and programming error can change the measured sum.

A negative weight needs an explicit representation, such as a difference of conductances, and corresponding sensing circuitry. A single passive conductance is not a negative weight.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Reliability is a measurement, not a slogan

Retention describes distinguishability after a stated time and temperature, with a defined read and failure criterion. Endurance is a cycle count under stated waveforms and failure criterion.

Separate cycle-to-cycle from device-to-device variation. Read margin depends on the sensing circuit and distributions, not merely two nominal resistance values.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Compare reliability only under matching protocols

Consider two hypothetical measurements, each on 100 cells. Test A reports 95 cells retaining distinguishable read currents after 1 hour at 85 °C; test B reports 98 cells after 1 hour at 25 °C. Both must specify read voltage and time, current thresholds, prior cycling and whether failed cells were excluded. Even with those records, different temperatures prevent treating the observed percentages as a controlled comparison of two materials.

For endurance, record the SET/RESET amplitudes, pulse widths, verify procedure and failure criterion. A short high-temperature retention measurement alone cannot establish 10-year retention at room temperature; an extrapolation requires a supported model, uncertainty and appropriate validation.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Applications and device requirements

Four uses: operations and device demands

Storage	Write state → read and decide Focus: read margin, retention, write endurance
Stateful logic	Read state → update state Focus: operations may consume writes
Offline inference	Program weights → repeated reads Focus: read accuracy, drift and converters
Online training	Read and compute → update weights Focus: update error, asymmetry and endurance

Conceptual flows; operations and peripheral costs depend on architecture.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Storage and selectors: the array sets the constraints

For digital storage, a read circuit must distinguish the programmed states at specified voltages and times. A large single-cell resistance ratio does not by itself guarantee a usable array read margin: wire resistance, sensing noise and currents through unselected cells also matter.

An access device can suppress unselected-path currents using gate control, as in 1T1R, or using a nonlinear two-terminal selector. Its leakage, drive current, switching speed and integration cost must be assessed together with the memory element; a selector is not automatically an ideal switch.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Stateful logic can require repeated writes

In stateful logic, a programmed device state participates in a logic operation and the result is stored by a subsequent state change. The precise voltage sequence and number of writes depend on the circuit and its logic convention. A reconfigurable circuit instead may write a configuration once and use it for many operations; do not assume each operation rewrites its configuration.

Suppose the **same cell** receives exactly k writes per operation, operations occur at N per second, and this rate is constant for T seconds. The cell accumulates NkT writes. For $k = 2$, $N = 10^3\,\mathrm{s}^{-1}$ and $T = 60\,\mathrm{s}$, this is 1.2×10^5 writes. If writes are spread across cells, sum each cell's actual writes instead. A write is not necessarily a complete SET/RESET cycle; endurance depends on the specified pulses and failure criterion.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Inference and training stress different properties

An analog crossbar can use programmed conductances to perform an approximate weighted sum. Offline inference programs weights before use: read noise, conductance drift, line resistance and ADC/DAC precision affect the result. Weight signs need an explicit representation, such as a differential pair.

Online training also updates conductances during learning. Update nonlinearity, asymmetry, quantization, stochasticity and write endurance can affect the training trajectory. Impact depends on the model, workload, mapping and compensation; neither inference nor training is automatically tolerant of every device imperfection.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

Temporal randomness differs from a device fingerprint

A stochastic switching device may produce different outcomes across repeated identical pulses. A random-number generator uses temporal variation; bias, serial correlation, readout and any post-processing must be characterized. Repeated switching also consumes endurance.

A physical unclonable function (PUF) instead aims to extract a reproducible device-specific response from spatial differences among devices. Its usefulness depends on stability under environmental changes, uniqueness across devices and measurement noise. Temporal randomness and spatial variation are different properties, even if a single device technology exhibits both.

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study

References and attribution

Jennifer Rupp, Daniele Ielmini, Ilia Valov (eds.), Resistive Switching: Oxide Materials, Mechanisms, Devices and Operations, Springer, 2022. DOI: 10.1007/978-3-030-42424-4.

Original educational synthesis by Lin Cing, licensed under CC BY 4.0.

https://github.com/xinhi6716/resistive-memory-self-study

Lin Cing
https://github.com/xinhi6716/resistive-memory-self-study